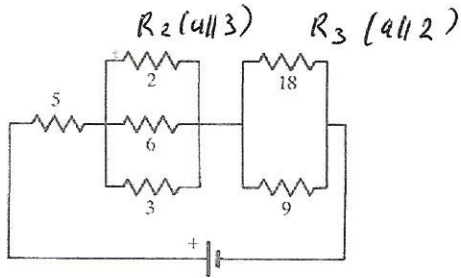


1. 6 resistors are connected to the 9 V battery as shown.



a. Find total resistance of this circuit.

$$\frac{1}{R_2} = \frac{1}{2} + \frac{1}{6} + \frac{1}{3} = 1 \quad R_2 = 1 \Omega \quad R_3 = \frac{1}{9} + \frac{1}{18} = \frac{3}{18} = \frac{1}{6} \quad R_3 = 6 \Omega$$

$$R_{total} = 5 + 1 + 6 = 12 \Omega$$

b. Find current through resistor 5 Ω

$$I_5 = I_{total} = \frac{V_{total}}{R_{total}} = \frac{9V}{12\Omega} = 0.75 A$$

c. Find voltage drop across 2 Ω resistor

$$V_2 = V_{R_2} = I_{total} R_2 = 0.75 \times 1 = 0.75 V$$

d. Find current through 6 Ω resistor.

$$I_6 = \frac{V_6}{6} = \frac{V_{R_2}}{6} = \frac{0.75}{6} = 0.125 A$$


d. Find voltage drop across 9 Ω resistor.

$$V_5 = I_5 \times 5 = 3.75 V \quad V_9 = V_{R_3} = V_{total} - V_5 - V_{R_2} = 9 - 3.75 - 0.75 = 4.5 V$$

e. Find current through 18 Ω resistor.

$$I_{18} = \frac{V_{18}}{18} = \frac{V_{R_3}}{18} = \frac{4.5}{18} = 0.25 A$$

A series-parallel combination circuit

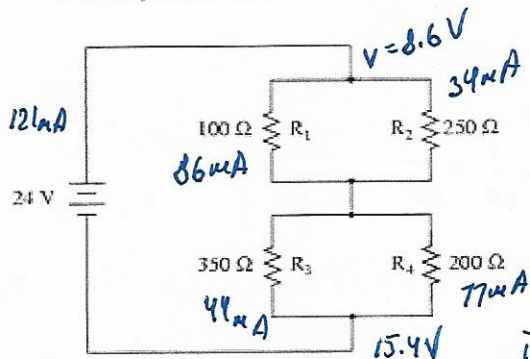


$$\frac{1}{100} + \frac{1}{250} = \frac{5}{500} + \frac{2}{500} = \frac{7}{500} \quad \frac{500}{7} \approx 71.4 \Omega$$

$$\frac{1}{200} + \frac{1}{350} = \frac{7}{1400} + \frac{4}{1400} = \frac{11}{1400} \quad \frac{1400}{11} \approx 127.3 \Omega$$

$$\frac{500}{7} + \frac{1400}{11} = \frac{5500 + 9800}{77} = \frac{15300}{77} \approx 198.7 \Omega$$

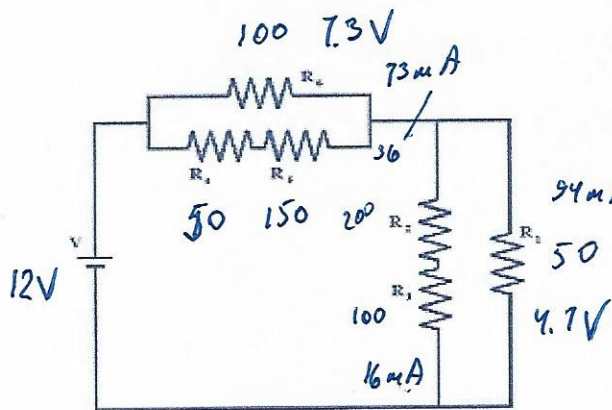
$$\bar{I} = \frac{24}{198.7} \approx 121 \text{ mA}$$



$$\frac{1}{100} + \frac{1}{200} + \frac{200}{3} \approx 66.7 \Omega$$

$$\frac{1}{50} + \frac{1}{300} = \frac{7}{300} \quad \frac{300}{7} \approx 42.9 \Omega$$
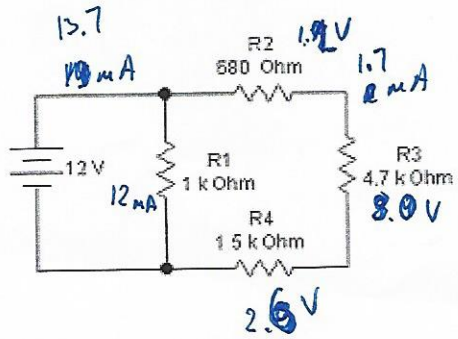
$$\frac{12}{109.6} \approx 109 \text{ mA}$$



$$680 + 4700 + 1500 = 6880 \Omega$$

$$\frac{1}{R_t} = \frac{1}{1000} + \frac{1}{6880} = 0.001145$$

$$R_t = 873 \Omega$$

~~873 \Omega~~ 873 \Omega

~~0.0137 A~~

$$I_t = \frac{12}{873} = 0.0137 A$$

V_{R_1}

$$I_{R_1} = \frac{12}{1000} = 0.012 A$$

$$I_{R_2} = I_{R_3} = I_{R_4} = I_t - I_{R_1}$$


$$= 0.0137 - 0.012$$

$$= 0.0017 A$$

$$V_{R_2} = I_{R_2} R_2$$

$$V_{R_3} = I_{R_3} R_3$$

$$V_{R_4} = I_{R_4} R_4$$

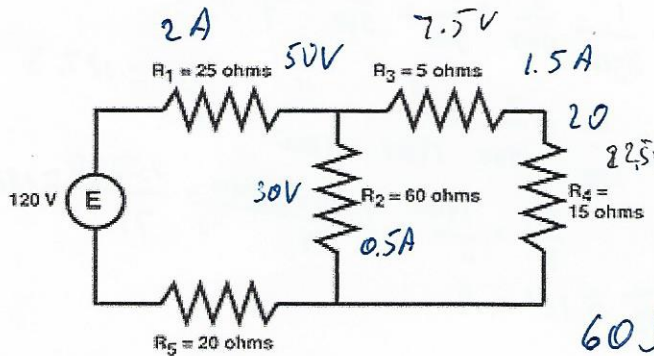

$$V_{R_3} = 2 \times 20 = 40V$$

$$V_{R_2} = 120 - 50 - 40 = 30V$$

$$V_{R_1} = 2 \times 25 = 50V$$

$$V_{R_3} = 2 \times 20 = 40V$$

Series-parallel

$$= 100 \times 4.5V$$

$$\frac{1}{20} + \frac{1}{60} = \frac{4}{60} \quad 15\Omega$$

$$R_t = 25 + 15 + 20 = 60\Omega$$

$$I_t = I_{R_1} = I_{R_5} = \frac{120}{60} = 2A$$


$$I_{R_2} = \frac{30}{60} = 0.5A$$

$$I_{R_3} = I_{R_4} = 2 - 0.5 = 1.5A$$

$$V_{R_3} = 1.5 \times 5 = 7.5$$


$$V_{R_4} = 1.5 \times 15 = 22.5V$$

$$V_{R_2} =$$

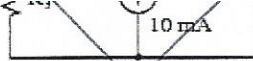


	R ₁	R ₂	R ₃	Total
V				
I				10 mA
R	4.7 kΩ	2.7 kΩ	3.9 kΩ	
P				

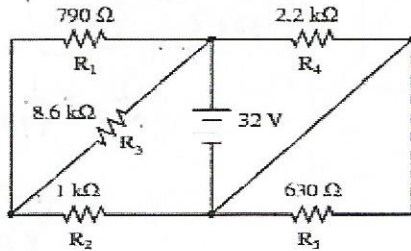Complete the table of values for this circuit:



	R ₁	R ₂	R ₃	R ₄	R ₅	Total
V		18.56 V		32	0	32
I		18.56 A		14.55 μA	0	33.11 mA
R	790 Ω	1 kΩ	8.6 kΩ	2.2 kΩ	630 Ω	966.4
P						

630 Ω shortcuted
2.2 kΩ

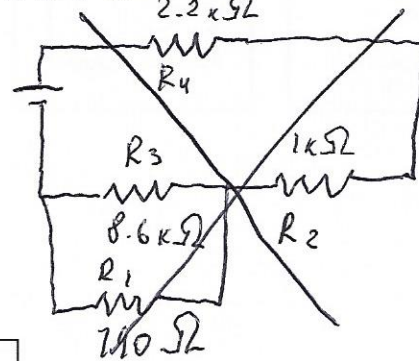

$$\frac{1}{8600} + \frac{1}{790} = 0.00138$$

$$\frac{1}{0.00138} = 723.5 \Omega$$

$$723.5 + 1000 = 1723.5 \Omega$$

$$\bar{I}_t = \frac{32}{966.4} = 0.03311$$

$$\bar{I}_{R_4} = \frac{32}{2200} = 0.01455 \text{ A}$$

$$\bar{I}_{R_2} = 33.11 - 14.55 = 18.56 \text{ A}$$

$$V_{R_2} = 18.56 \times 10^{-3} \times 1000 = 18.56 \text{ V}$$

$$V_{R_1} = V_{R_3} = 32 - 18.56 = 13.44 \text{ V}$$

$$\bar{I}_{R_1} = \frac{13.44}{790}$$

$$\bar{I}_{R_3} = \frac{13.44}{8600}$$

$$\frac{1}{R_t} = \frac{1}{2200} + \frac{1}{1723.5} = 0.001035$$

$$R_t = \frac{1}{0.001035} = 966.4 \Omega$$

$$R_3 + R_4 = 600 \Omega$$

$$\frac{1}{(R_1 R_3 R_4)} = \frac{1}{600} + \frac{1}{1000} = 0.00267 \quad (R_1 R_3 R_4) = 428.18 \Omega$$

$$R_t = 500 + 375 = 875 \Omega$$

$$\bar{I}_t = \bar{I} R_2 = \frac{11}{875} = 12.57 \text{ mA}$$

$$V_{R_2} = 500 \times 0.01257 = 6.3 \text{ V}$$

$$\bar{I}_{R_2 R_3} = 12.57 - 4.7$$

$$= 7.87 \text{ mA}$$

$$V_{R_3} = 7.87 \times 150 \times 10^{-3}$$

$$V_{R_4} = 0.00787 \times 450$$

$$V_{R_1} = 11 - 6.3 = 4.7 \text{ V} \quad \bar{I}_{R_1} = \frac{4.7}{1000} = 4.7 \text{ mA}$$

