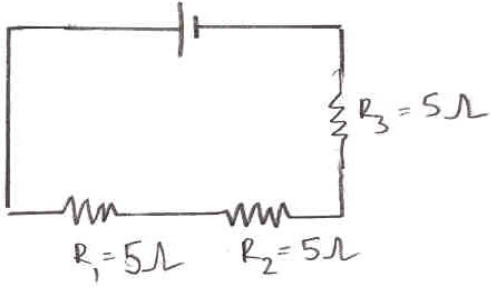


Resistance in Series and Parallel Worksheet

 <p style="margin-top: 10px;">$R_{\text{equivalent}} = R_1 + R_2 + R_3 =$</p>	<p>Resistors in parallel</p> $\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} =$
---	---

1. Find the equivalent resistance of these series circuits (in Ω) :

<p>a) $R_1 = 100 \Omega$ $R_2 = 20 \Omega$ $R_3 = 55 \Omega$</p>	<p>b) $R_1 = 7500 \Omega$ $R_2 = 1.5 \text{ k}\Omega$ $R_3 = 25 \Omega$</p>	<p>c) $R_1 = 0.1 \Omega$ $R_2 = 0.2 \Omega$ $R_3 = 50 \text{ m}\Omega$</p>
---	--	---

2. Find the equivalent resistance of these parallel circuits (in Ω) :


<p>a) $R_1 = 100 \Omega$ $R_2 = 20 \Omega$ $R_3 = 55 \Omega$</p>	<p>b) $R_1 = 7500 \Omega$ $R_2 = 1.5 \text{ k}\Omega$ $R_3 = 25 \Omega$</p>	<p>c) $R_1 = 0.1 \Omega$ $R_2 = 0.2 \Omega$ $R_3 = 50 \text{ m}\Omega$</p>
---	--	---

3. The same two equations above work for any number of resistors in a circuit. If a fourth resistor is added ($R_4 = 85 \Omega$), find the equivalent resistance in 1a) and 2a).


<p>1a)</p>	<p>2a)</p>
------------	------------

4. Calculate the equivalent resistance of the following circuits:


a) $R_1 = 5 \Omega$ $R_2 = 10 \Omega$

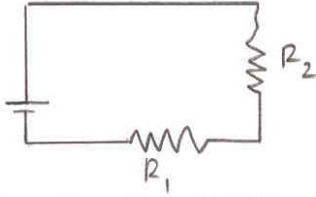


b) $R_1 = R_2 = R_3 = 1.5 \Omega$

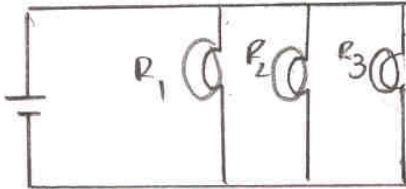

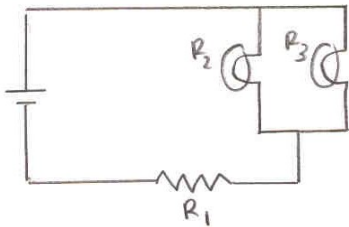c) $R_1 = 12 \Omega$ $R_2 = 5 \Omega$ $R_3 = 8 \Omega$



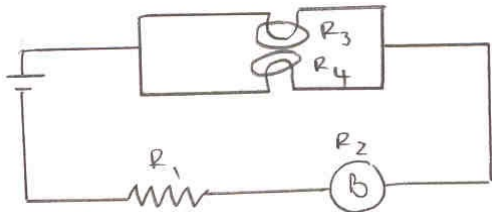d) $R_1 = 1 \Omega$ $R_2 = 2 \Omega$ $R_3 = 3 \Omega$ $R_4 = 4 \Omega$



5. Three light bulbs of 4Ω resistance each are in a parallel with a $9V$ power supply. Draw the circuit, and find the current.

6. Three identical buzzers are in parallel with a $110 V$ power supply. The circuit has a current of $1.5 A$. Draw the circuit. Find the resistance of one buzzer.