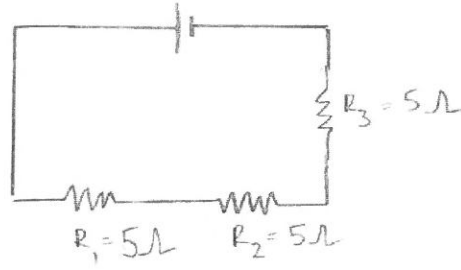


Resistance in Series and Parallel Worksheet

 <p style="margin-top: 20px;">$R_{\text{equivalent}} = R_1 + R_2 + R_3 = 15 \Omega$</p>	<p>Resistors in parallel</p> $R = \frac{5}{3} = 1.67 \Omega$ $\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{5} + \frac{1}{5} + \frac{1}{5} = \frac{3}{5}$
---	---

1. Find the equivalent resistance of these series circuits (in Ω) :

<p>a) $R_1 = 100 \Omega$ $R_2 = 20 \Omega$ $R_3 = 55 \Omega$</p> $R = 100 + 20 + 55 = 175 \Omega$	<p>b) $R_1 = 7500 \Omega$ $R_2 = 1.5 \text{ k}\Omega$ $R_3 = 25 \Omega$</p> $R = 7500 + 1500 + 25 = 9025 \Omega$	<p>c) $R_1 = 0.1 \Omega$ $R_2 = 0.2 \Omega$ $R_3 = 50 \text{ m}\Omega$</p> $R = 0.1 + 0.2 + 0.05 = 0.35 \Omega$
--	---	--

2. Find the equivalent resistance of these parallel circuits (in Ω) :


<p>a) $R_1 = 100 \Omega$ $R_2 = 20 \Omega$ $R_3 = 55 \Omega$</p> $\frac{1}{R} = \frac{1}{100} + \frac{1}{20} + \frac{1}{55} = \frac{43}{550}$ $R = \frac{550}{43} = 12.8 \Omega$	<p>b) $R_1 = 7500 \Omega$ $R_2 = 1.5 \text{ k}\Omega$ $R_3 = 25 \Omega$</p> $\frac{1}{R} = \frac{1}{7500} + \frac{1}{1500} + \frac{1}{25} = \frac{51}{1250}$ $R = \frac{1250}{51} = 24.5 \Omega$	<p>c) $R_1 = 0.1 \Omega$ $R_2 = 0.2 \Omega$ $R_3 = 50 \text{ m}\Omega$</p> $\frac{1}{R} = \frac{1}{0.1} + \frac{1}{0.2} + \frac{1}{0.05} = 35$ $R = \frac{1}{35} = 0.03 \Omega$
---	---	--

3. The same two equations above work for any number of resistors in a circuit. If a fourth resistor is added ($R_4 = 85 \Omega$), find the equivalent resistance in 1a) and 2a).

<p>1a)</p> $175 + 85 = 260 \Omega$	<p>2a)</p> $\frac{1}{100} + \frac{1}{20} + \frac{1}{55} + \frac{1}{85} = \frac{841}{9350} = \frac{1}{R}$ $R = \frac{9350}{841} = 11.1 \Omega$
------------------------------------	---


4. Calculate the equivalent resistance of the following circuits:

a) $R_1 = 5 \Omega$ $R_2 = 10 \Omega$

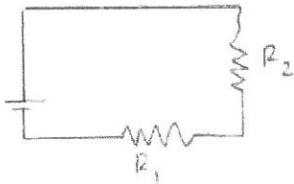


$$R = R_1 + R_2 = 15 \Omega$$

b) $R_1 = R_2 = R_3 = 1.5 \Omega$

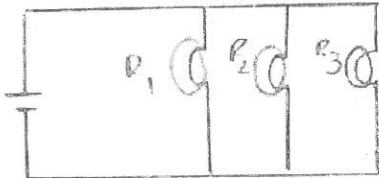

$$\frac{1}{R} = \frac{1}{1.5} + \frac{1}{1.5} + \frac{1}{1.5} = \frac{3}{1.5} = 2 \quad R = \frac{1}{2} = 0.5 \Omega$$

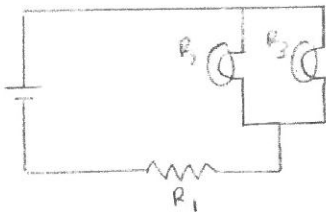
c) $R_1 = 12 \Omega$ $R_2 = 5 \Omega$ $R_3 = 8 \Omega$



$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{5} + \frac{1}{8} = \frac{13}{40} \quad R = \frac{40}{13} = 3.1 \Omega$$

$$R_{total} = R_1 + R = 12 + 3.1 = 15.1 \Omega$$

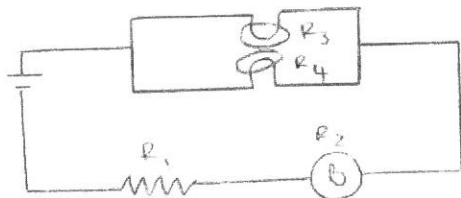
d) $R_1 = 1 \Omega$ $R_2 = 2 \Omega$ $R_3 = 3 \Omega$ $R_4 = 4 \Omega$



$$\frac{1}{R} = \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{3} + \frac{1}{4} = \frac{7}{12} \quad R = \frac{12}{7} = 1.7 \Omega$$

$$R_{total} = R_1 + R_2 + R = 1 + 2 + 1.7 = 4.7 \Omega$$

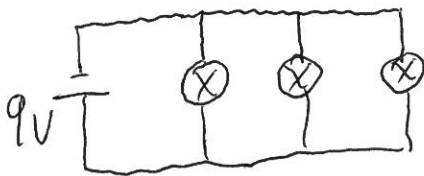5. Three light bulbs of 4Ω resistance each are in a parallel with a $9V$ power supply. Draw the circuit, and find the current.




$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4} + \frac{1}{4} = \frac{3}{4}$$

$$R = \frac{4}{3} = 1.3 \Omega$$

$$I = \frac{V}{R} = \frac{9}{1.3} = 6.9 A$$

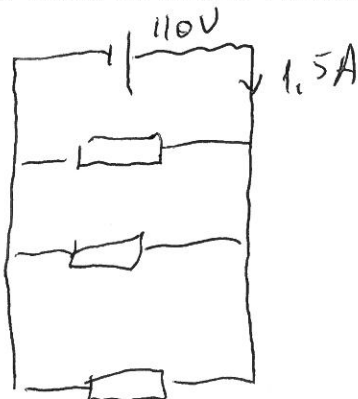6. Three identical buzzers are in parallel with a $110 V$ power supply. The circuit has a current of $1.5 A$. Draw the circuit. Find the resistance of one buzzer.



$$R_{total} = \frac{V}{I} = \frac{110}{1.5} = 73.3 \Omega$$

$$R = 3 \times R_{total} = 3 \times \frac{110}{1.5} = 220 \Omega$$