

Name \_\_\_\_\_ Date \_\_\_\_\_ Period \_\_\_\_\_

# Worksheet: Circuits & Ohm's Law

## CHAPTER 35: SERIES AND PARALLEL CIRCUITS

**Directions:** Answer the following questions based on reading from Chapter 23 (pgs. 531-550) and/or from notes in class.

**Equations:**

$$\text{Electric Potential} = \frac{\text{electric potential energy}}{\text{amount of charge}} \quad 1 \text{ volt} = \frac{1 \text{ joule}}{\text{coulomb}}$$

### GENERAL EQUATIONS

$$I = \frac{V}{R} \quad \boxed{\text{Current} = \frac{\text{voltage}}{\text{resistance}}} \quad \boxed{\text{Amperes} = \frac{\text{volts}}{\text{ohms}}} \quad P = IV$$

### SERIES CIRCUITS


$$I = \frac{I_S}{R} \quad R = R_A + R_B + \dots \quad V_S = V_1 + V_2 + V_3 + V_4 + \dots$$

### PARALLEL CIRCUITS

$$I_A = \frac{V}{R_A} \quad I = I_A + I_B + I_C \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_S = V_1 = V_2 = V_3 = V_4 + \dots$$


### ELECTRICAL CIRCUIT SYMBOLS

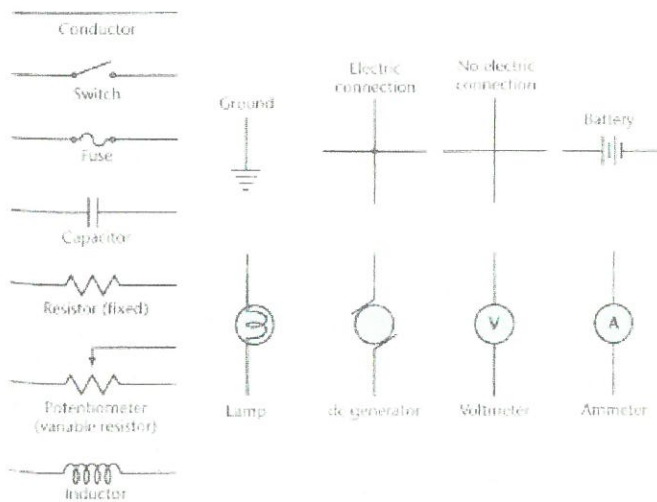

### QUESTIONS:

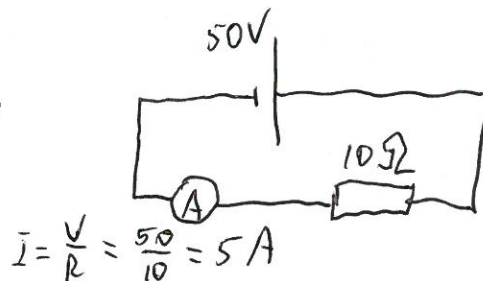1. Draw a **circuit schematic** (diagram) to include a **50.0 V** battery, an **ammeter**, and a resistance of **10.0 Ω** in series.

- What is the reading on the **ammeter**?
- In which **direction** is the **current** flowing?




clockwise

2. How much **current** flows through a radio speaker that has a resistance of  $4.0 \Omega$  when  $16 \text{ V}$  is impressed across the speaker?

$$\bar{I} = \frac{16}{4} = 4 \text{ A}$$

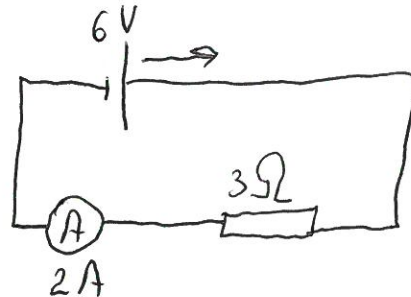3. Draw a **circuit diagram** of the circuit described in the question above. Include a  $6 \text{ V}$  battery, an **ammeter** (labeled with value of **current**), and a **resistance** of  $3.0 \Omega$  (the speaker). Also label the **direction** of the conventional (+) current.




$$\bar{I} = \frac{6}{3} = 2 \text{ A}$$

4. The following questions pertain to the circuit diagramed to the right.

a. **Lamp A** reads a voltage of  $12 \text{ V}$ . What is the voltage of **lamp B**?

$$12 \text{ V}$$

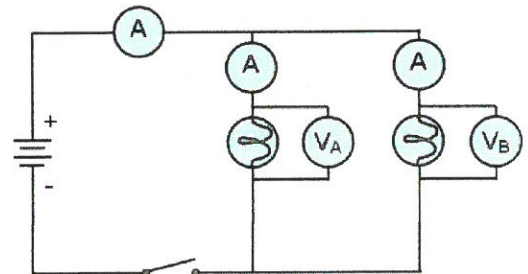

b. If the ammeters on both branches read the same amount, what does this tell you about the **resistance** of the two branches?

It is the same.


c. If the current flowing in the first branch was  $4.0 \text{ A}$  and  $6.0 \text{ A}$  in the second branch, what would the **total current** in the circuit be?

$$4 + 6 = 10 \text{ A}$$

5. Draw a series **circuit diagram** showing a  $6.0 \text{ V}$  battery, a **resistor**, & an **ammeter** reading of  $2.0 \text{ A}$ .


a. Label: the size of the resistor, the direction of conventional current, the (+) and (-) terminals of the battery.

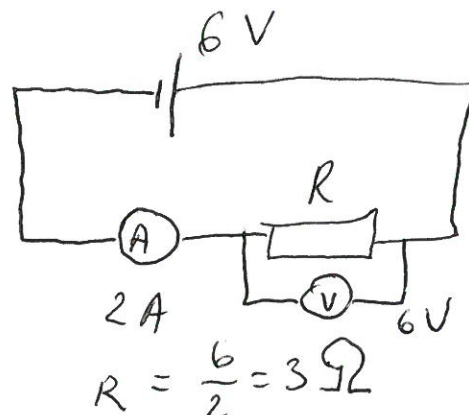b. Add a voltmeter to your diagram and indicate the **potential difference** across the resistor.



$$R = \frac{6}{2} = 3 \Omega$$

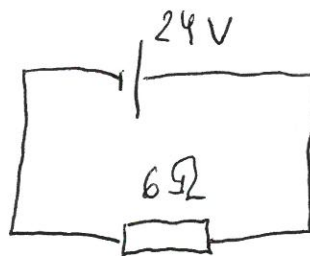6. Draw a **circuit diagram** showing a heater with a resistance of  $6\ \Omega$ , and a potential difference source of  $24.0\ \text{V}$ .



a. Calculate the **current** through the resistance

$$I = \frac{24}{6} = 4\ \text{A}$$


b. What **thermal energy** is supplied by the heater in 10 seconds? (HINT- use the equation  $E = I^2 R t$  to determine energy)

$$E = 4^2 \times 6 \times 10 = 960\ \text{Jt}$$

7. Use the **circuit diagram** to the right to answer the following questions.

a. What is the **current** flowing through this series circuit if the total resistance is  $20\ \Omega$ ?

$$I = \frac{24}{20} = 1.2\ \text{A}$$

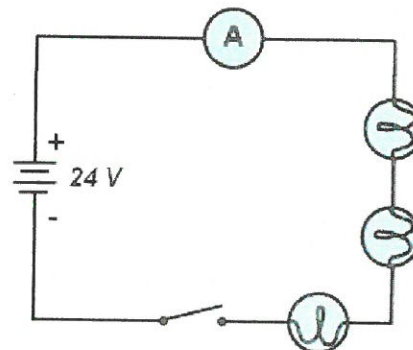

b. What would the **voltage** across each of the three bulbs be? What could you say about the **brightness** of each of the bulbs?

$$V = \frac{24}{3} = 8\ \text{V}$$

c. If two of the bulbs had a total resistance of  $15\ \Omega$ , what would the **resistance** of the third bulb be?


$$R_{\text{total}} = 20\ \Omega \quad R_3 = 20 - 15 = 5\ \Omega$$

d. What would be the **current** flowing through the circuit be if the voltage source was  $6.0\ \text{V}$ , and each of the lamps had a resistance of  $2\ \Omega$ ?

$$R_{\text{total}} = 2 \times 3 = 6\ \Omega$$

$$I = \frac{6}{6} = 1\ \text{A}$$

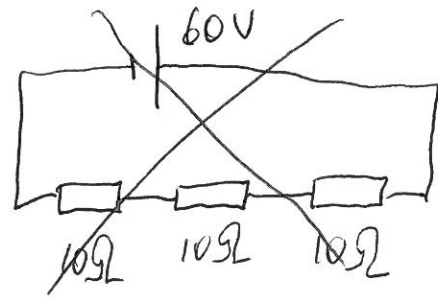8. Draw a **circuit diagram** showing three  $10\ \Omega$  resistors connected in parallel and placed across a  $60.0\ \text{V}$  battery.



a. What is the **equivalent resistance** of the parallel circuit?

$$10 \div 3 = 3.33\ \Omega$$


$$R_t = \cancel{10 \times 3 = 30\ \Omega}$$

b. What is the **current** through the **entire circuit**?


$$I = \frac{60}{\cancel{10/3}} = \cancel{2\ \text{A}} = 18\ \text{A}$$

c. What is the **current** through each **branch** of the circuit?

$$18 \div 3 = 6\ \text{A}$$

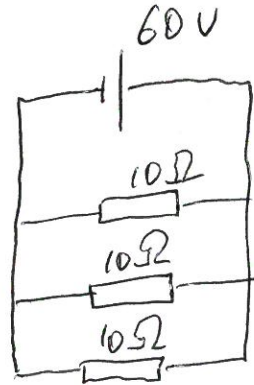

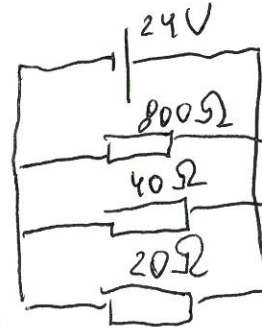9. Draw a **circuit diagram** showing the following: a  $800.0\ \Omega$  resistor, a  $40\ \Omega$  resistor, and a  $20\ \Omega$  resistor connected in parallel and connected across a  $24.0\ \text{V}$  battery.



a. What is the **equivalent resistance** of the parallel circuit?

$$\frac{1}{R} = \frac{1}{800} + \frac{1}{40} + \frac{1}{20} = \frac{1+20+40}{800} = \frac{61}{800} \quad R = \frac{800}{61}$$


b. What is the **current** through the **entire circuit**?  $= 13.1\ \text{A}$

$$I = \frac{24}{\frac{800}{61}} = \frac{24 \times 61}{800} = 1.8\ \text{A}$$

c. What is the **current** through each **branch** of the circuit?

$$\frac{24}{800} = 0.03\ \text{A} \quad \frac{24}{40} = 0.6\ \text{A} \quad \frac{24}{20} = 1.2\ \text{A}$$

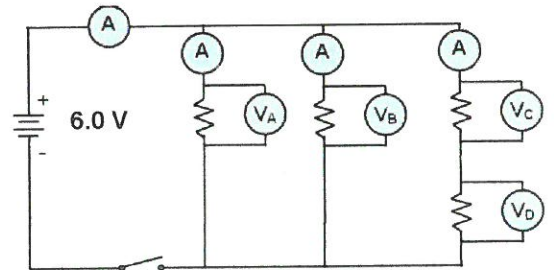10. Answer the following questions about the circuit to the right.



a. What do each of the 4 **voltmeters** read?

$$V_A = V_B = 6\ \text{V}$$

$$V_C = V_D = \frac{6}{2} = 3\ \text{V}$$

b. If each of the resistors are identical, and the **total current** flowing through this parallel circuit is  $12.0\ \text{A}$ , what is the **total resistance** of this circuit?

$$R = \frac{V}{I} = \frac{6}{12} = 0.5\ \Omega$$